


# Lightbulbs

## Series v. Parallel

$$P = \text{Watts} = IV = I^2 R = \frac{V^2}{R}$$

- When you look at a 100W lightbulb, here's what it is telling you: "I am 100W if you run 120V of electricity through me". All American lightbulbs have their wattage based on 120V coming from the wall

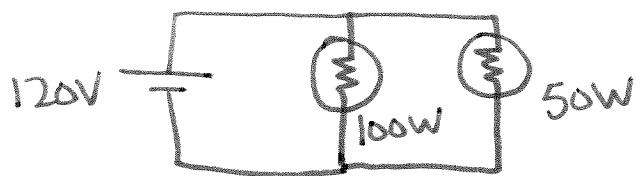Lightbulbs in <sup>Parallel</sup> (The way your house - and mine - are wired)



- You and I know (and so does your grandma for that matter) that a 100W bulb is brighter than a 50 W bulb
- But does grandma know how to determine the resistance of the bulbs based on the above information? (only if she's a physics teacher)

$$R = \frac{V^2}{P}$$

$$R_{100W} = \frac{(120V)^2}{100W} = 144\Omega$$

$$R_{50W} = \frac{(120V)^2}{50W} = 288\Omega$$


- No big surprise there, the high watt bulb has low resistance to allow more current through it than the 50W bulb

Bright!  $\rightarrow I_{100W} = \frac{V}{R} = \frac{120V}{144\Omega} = 0.833 \text{ Amps}$

dim  $\rightarrow I_{50W} = \frac{120V}{288\Omega} = 0.417 \text{ Amps}$

- The electric company loves 100W bulbs.  
Do you see why? Remember,  $I = \frac{Q}{\text{time}}$ . Bigger The I, the bigger the Q, The bigger the \$!
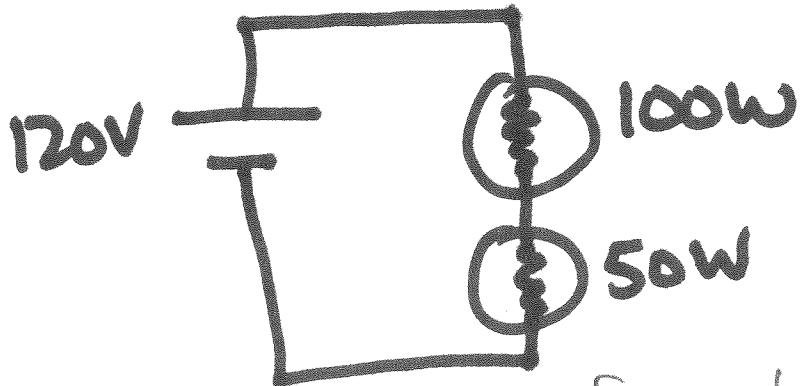
## Series lightbulb (Horror's of Horrors! 😱)



- Resistance is same for each individual bulb, but the resistance of the series is  $R_{100W} + R_{50W}$

$$144\Omega + 288\Omega = 432\Omega$$

- Recall that in series circuits, only one current may flow (an infinite amount of currents may flow in parallel!)

$$V = IR$$

$$120V = I(432\Omega)$$

$$I = 0.278 \text{ Amps}$$

Okay grandma, hang on now!

You only got 0.278 Amps flowing through your two lightbulbs now. Let's figure out the wattage now

$$P_{100W} = I^2 R = (0.278)^2 (144\Omega)$$

$$P_{100W} = 11.13 \text{ Watts}$$

$$P_{50W} = I^2 R = (0.278)^2 (288\Omega)$$

$$P_{50W} = 22.26 \text{ Watts}$$

You'd have to be a dim bulb not to see that the 50W bulb is going to outshine its 100W friend!

## Why?

- Putting them in series forces them to share the same current.

$$P = I^2 R$$

and since  $R_{50W} > R_{100W}$ , then  $P_{50W} > P_{100W}$

- Left in parallel, they would draw the individual currents they would need to glow as nature intended them.